

# Reducing radiated EMI in WLED drivers

By Jeff Falin

Senior Applications Engineer

Most mobile phones use white LEDs (WLEDs) as the backlight for their displays. Li-Ion batteries with an output range of 2.7 to 4.2 V are the most common power source for mobile phones. Since several WLEDs in series, each with forward voltages around 3.6 V, are typically used for the backlight, the backlight driver must provide a voltage higher than the Li-Ion range. Therefore, an inductive boost converter is a common power-supply topology for WLED drivers. Figure 1 shows a typical backlight-driver solution that uses the TPS61161 to drive ten LEDs in series.


All inductive switching converters cause radiated electromagnetic interference (EMI) that is directly proportional to output power. As the size of mobile phone displays increases to accommodate more features, the backlight driver's increased output power results in more EMI. Factors at each design step, from driver-IC selection to board layout, impact the WLED driver's EMI. Therefore, minimizing the WLED backlight driver's radiated EMI so that it does not affect other systems is a major concern for manufacturers of both the backlight driver IC and the mobile phone.

Radiated EMI is caused by induced electric fields where capacitors store their energy, and induced magnetic fields where inductors store their energy. The electric-field

strength of a capacitor is directly proportional to its capacitance and the voltage across its terminals. The capacitance is inversely proportional to the distance between the terminals. Ideally, the IC and components are laid out on the board to minimize the undesired (often called "parasitic") capacitance. Such capacitance can be created, for example, by a large metal trace or plane on top of a ground trace or plane. Likewise, an inductor's magnetic-field strength is directly proportional to its inductance value and the current flowing through it. The inductance value is directly proportional to the wire or trace length. The board ideally is laid out to minimize parasitic inductance created by long wires, loops, and traces; and shielded inductors are used on the PCB itself. Moreover, the rate of change of the voltages across and the currents through these parasitic components directly impacts their field strengths. Key methods of reducing EMI are to minimize the size of and interaction between these parasitic components and to reduce their voltages and current ramp rates.

The circuit designer and IC-layout engineer are responsible for minimizing the parasitic inductances and capacitances that occur at high frequencies (greater than 300 MHz) and/or for managing voltage and current ramp rates inside the IC. Otherwise, the IC itself will generate

Figure 1. TPS61161 backlight driver

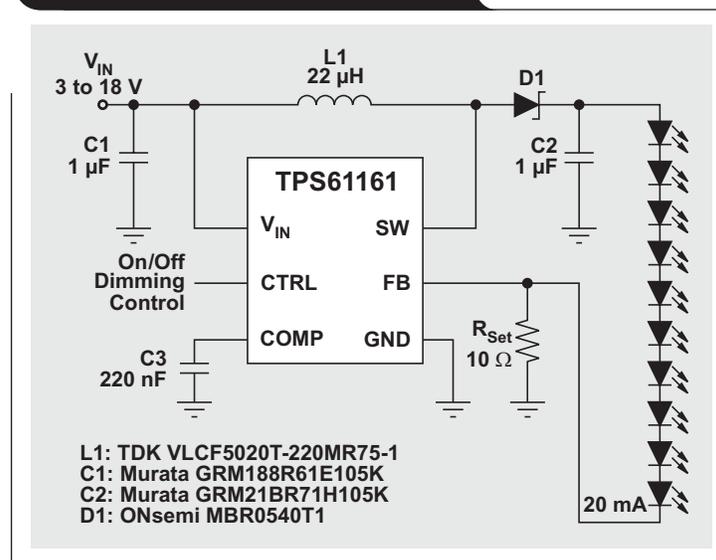



**all-electronics.de**

ENTWICKLUNG. FERTIGUNG. AUTOMATISIERUNG



Entdecken Sie weitere interessante Artikel und News zum Thema auf all-electronics.de!


**Hier klicken & informieren!**



EMI. Consider Figure 2, which shows the drain voltage,  $V_{DS}$ , of the TPS61161's internal NMOS FET (i.e., the switch node) as the FET turns on. The blue trace is from a test board with beta TPS61161 silicon that has a commonly used high-speed gate drive. The red trace shows the same node on the same test board but with the final TPS61161 silicon that has TI's dual-slope switching technology. This technology controls the switch node's slope on the falling edge (i.e.,  $dv/dt$ ) in two steps. When the internal power FET first turns on, there is a large current spike. During the first step of a dual-slope FET compared to a normal FET, the  $dv/dt$  is slowed to reduce the amplitude of the current spike and the EMI that results primarily from parasitic inductance. During the second step, the switch FET returns to its normal, faster  $dv/dt$  to minimize the switching losses that would otherwise occur.


To measure the far-field EMI from a battery-powered evaluation module (TPS61161EVM-243), an IC with a traditional switch (shown in red in Figure 3) and an IC with a dual-slope switch (shown in green) were used in the same test environment. The black curve shows the noise floor of the measurement, and the 850-MHz spike is


**Figure 2. Switch node ( $V_{DS}$  of NMOS FET) of TPS61161's WLED driver**

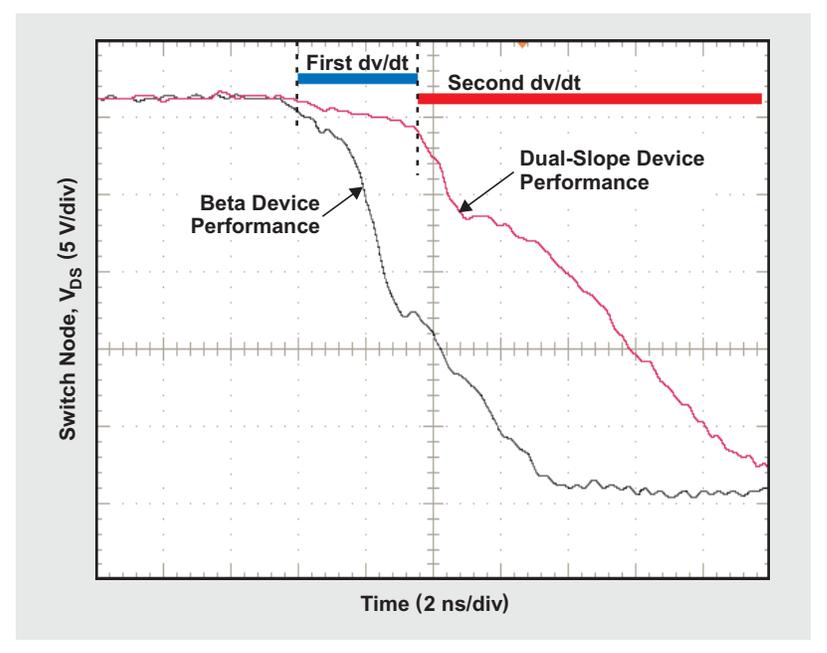


from a spurious GSM signal. It is clear that the dual-slope switching technology reduced the EMI in the 400-MHz range by 10 dB $\mu$ V/m.

**Figure 3. TPS61161's EMI measurements with traditional switch and dual-slope switch**

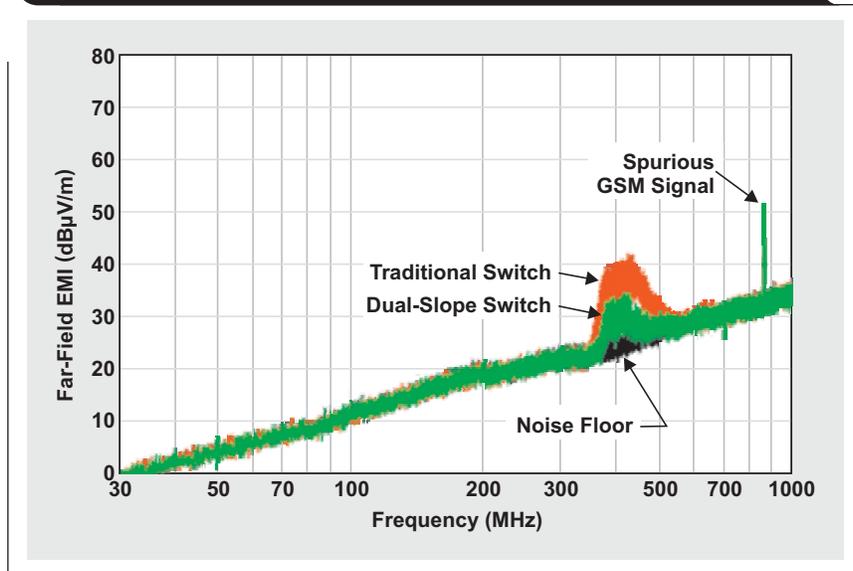

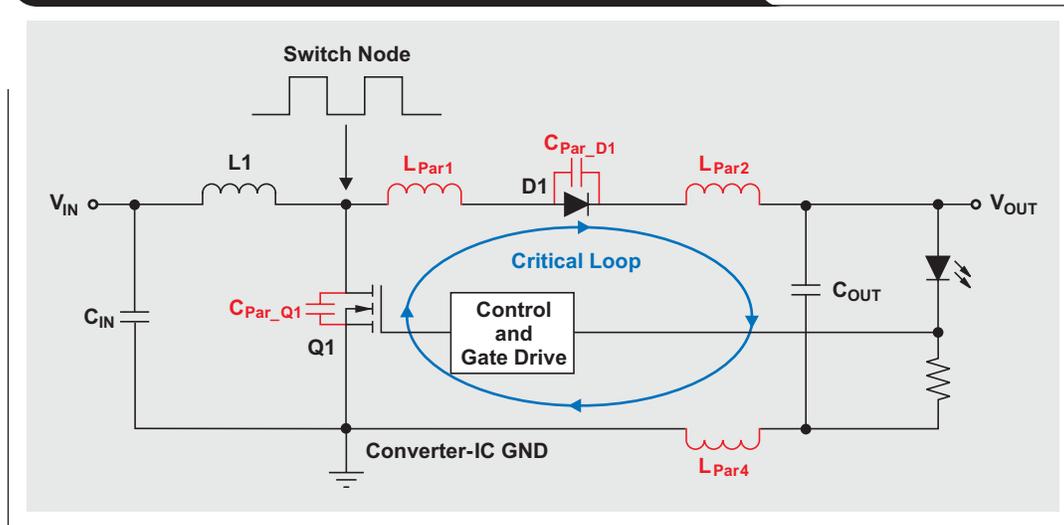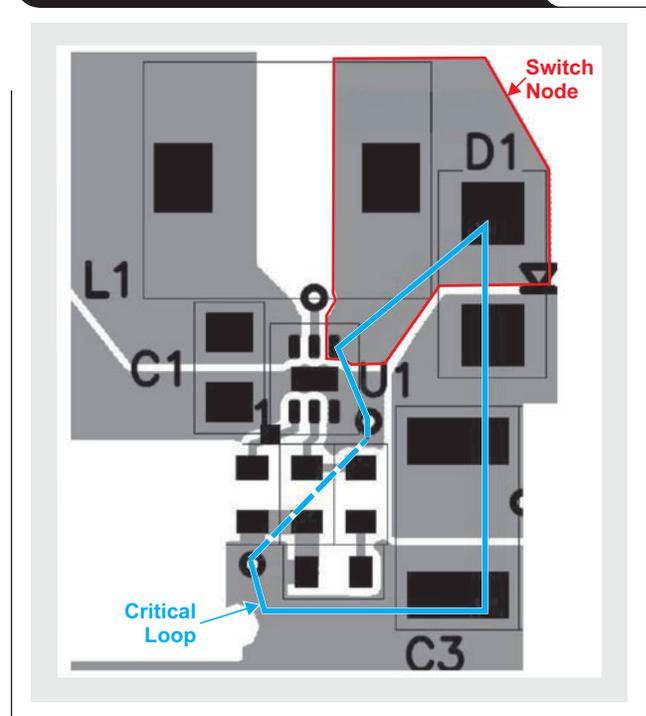**Figure 4. Schematic of boost-converter-based WLED driver**

At lower frequencies, the parasitic inductance and capacitance of the PCB's traces and planes are the primary contributors to EMI. Figure 4 shows the schematic for a boost-converter-based WLED driver. The loop created by the parasitic capacitance of Q1 and D1 and the parasitic inductance of the board traces conducts current when switches D1 and Q1 turn on and off. When switch Q1 turns off, inductor L1 is fully charged and ready to continue the current flow. Since the only available element through which current can continue to flow is D1, the inductor voltage quickly switches from GND to  $V_{OUT}$ , which causes ringing due to the parasitics. The resonance point of the parasitic inductance and capacitance can sometimes be seen on the oscilloscope as ringing at the resonant frequency. In addition to the parasitic capacitance of Q1 and D1, ground planes and the traces over/under them also contribute to parasitic capacitance. A commonly overlooked type of parasitic capacitance is that formed by the switch node—with its large  $dv/dt$ —and the ground plane underneath. Figure 5 shows a poor PCB layout that uses the TPS61161, where L1 is the inductor, D1 is the diode, U1 is the TPS61161 controller, C1 is the input capacitor, and C3 and C4 are the output capacitors. The critical loop, highlighted in blue, is long; and there is a large ground plane underneath the large pad for L1 that serves as the high-speed switch node (not shown).

**Figure 5. Poor PCB layout with TPS61161**

**Figure 6. Improved PCB layout with TPS61161**

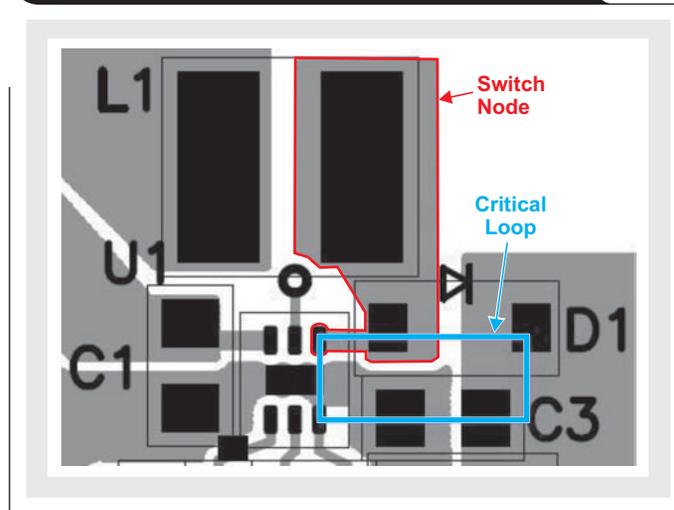


Figure 6 shows the TPS61161 evaluation module with the same components as in Figure 5 but with a smaller switch node, no ground plane underneath, and more compact part placement to reduce the length of the critical loop (shown in blue).

Figure 7 shows the near-field EMI measurements from two battery-powered test boards, one with poor layout and the other with improved layout. The tests were conducted under identical conditions with the same inductor and the TPS61161 (final silicon). Clearly, an improved board layout that minimizes parasitic board capacitance and inductance reduces EMI across multiple frequencies.

A switching converter’s EMI cannot be completely eliminated. However, with careful IC and passive-component selection as well as good board-layout techniques, EMI can be reduced to acceptable levels.

**Reference**

For more information related to this article, you can download an Acrobat® Reader® file at [www-s.ti.com/sc/techlit/litnumber](http://www-s.ti.com/sc/techlit/litnumber) and replace “litnumber” with the **TI Lit. #** for the materials listed below.

**Document Title**


**TI Lit. #**

1. “White LED Driver With Digital and PWM Brightness Control in 2mm × 2mm QFN Package for up to 10 LEDs in Series,” TPS61160/61 Data Sheet. . . . . slvs791

**Related Web sites**

[power.ti.com](http://power.ti.com)  
[www.ti.com/sc/device/TPS61161](http://www.ti.com/sc/device/TPS61161)

**Figure 7. TPS61161’s EMI measurements with poor and improved layouts**

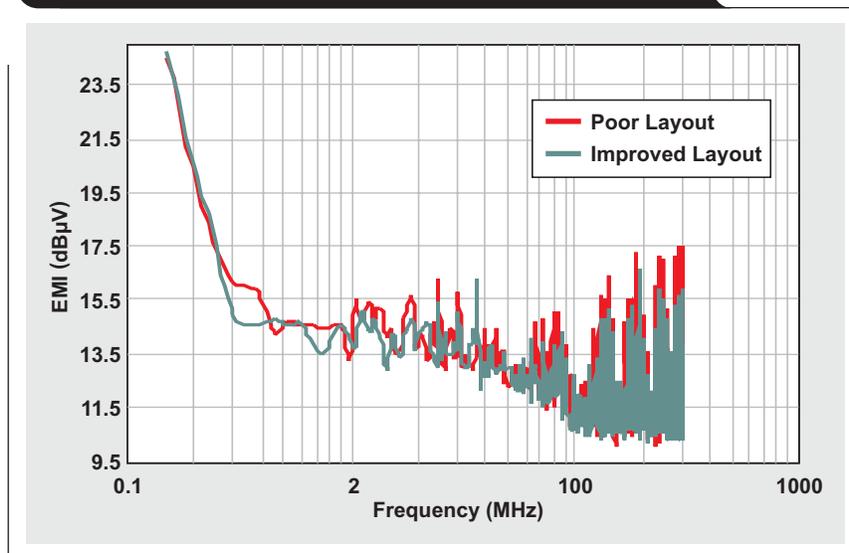

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

| <b>Products</b>                |  | <b>Applications</b> |  |
|--------------------------------|--|---------------------|--|
| Amplifiers                     | <a href="http://amplifier.ti.com">amplifier.ti.com</a>             | Audio               | <a href="http://www.ti.com/audio">www.ti.com/audio</a>                   |
| Data Converters                | <a href="http://dataconverter.ti.com">dataconverter.ti.com</a>     | Automotive          | <a href="http://www.ti.com/automotive">www.ti.com/automotive</a>         |
| DLP® Products                  | <a href="http://www.dlp.com">www.dlp.com</a>                       | Broadband           | <a href="http://www.ti.com/broadband">www.ti.com/broadband</a>           |
| DSP                            | <a href="http://dsp.ti.com">dsp.ti.com</a>                         | Digital Control     | <a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a> |
| Clocks and Timers              | <a href="http://www.ti.com/clocks">www.ti.com/clocks</a>           | Medical             | <a href="http://www.ti.com/medical">www.ti.com/medical</a>               |
| Interface                      | <a href="http://interface.ti.com">interface.ti.com</a>             | Military            | <a href="http://www.ti.com/military">www.ti.com/military</a>             |
| Logic                          | <a href="http://logic.ti.com">logic.ti.com</a>                     | Optical Networking  | <a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a> |
| Power Mgmt                     | <a href="http://power.ti.com">power.ti.com</a>                     | Security            | <a href="http://www.ti.com/security">www.ti.com/security</a>             |
| Microcontrollers               | <a href="http://microcontroller.ti.com">microcontroller.ti.com</a> | Telephony           | <a href="http://www.ti.com/telephony">www.ti.com/telephony</a>           |
| RFID                           | <a href="http://www.ti-rfid.com">www.ti-rfid.com</a>               | Video & Imaging     | <a href="http://www.ti.com/video">www.ti.com/video</a>                   |
| RF/IF and ZigBee®<br>Solutions | <a href="http://www.ti.com/lprf">www.ti.com/lprf</a>               | Wireless            | <a href="http://www.ti.com/wireless">www.ti.com/wireless</a>             |

Mailing Address: Texas Instruments  
Post Office Box 655303  
Dallas, Texas 75265

# TI Worldwide Technical Support

---

## Internet

### TI Semiconductor Product Information Center Home Page

[support.ti.com](http://support.ti.com)

### TI Semiconductor KnowledgeBase Home Page

[support.ti.com/sc/knowledgebase](http://support.ti.com/sc/knowledgebase)

## Product Information Centers

|                 |                |  |
|-----------------|----------------|--|
| <b>Americas</b> | Phone          | +1(972) 644-5580   |
| <b>Brazil</b>   | Phone          | 0800-891-2616  |
| <b>Mexico</b>   | Phone          | 0800-670-7544  |
|                 | Fax            | +1(972) 927-6377   |
|                 | Internet/Email | <a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a> |

### Europe, Middle East, and Africa

|                    |                                      |
|--------------------|--------------------------------------|
| Phone              |                                      |
| European Free Call | 00800-ASK-TEXAS<br>(00800 275 83927) |
| International      | +49 (0) 8161 80 2121                 |
| Russian Support    | +7 (4) 95 98 10 701                  |

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

|          |  |
|----------|--|
| Fax      | + (49) (0) 8161 80 2045  |
| Internet | <a href="http://support.ti.com/sc/pic/euro.htm">support.ti.com/sc/pic/euro.htm</a> |

### Japan

|                |               |  |
|----------------|---------------|--|
| Fax            | International | +81-3-3344-5317  |
|                | Domestic      | 0120-81-0036   |
| Internet/Email | International | <a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a> |
|                | Domestic      | <a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>                             |

### Asia

|               |  |
|---------------|--|
| Phone         |  |
| International | +91-80-41381665  |
| Domestic      | <u>Toll-Free Number</u>  |
| Australia     | 1-800-999-084  |
| China         | 800-820-8682   |
| Hong Kong     | 800-96-5941  |
| India         | 1-800-425-7888   |
| Indonesia     | 001-803-8861-1006  |
| Korea         | 080-551-2804   |
| Malaysia      | 1-800-80-3973  |
| New Zealand   | 0800-446-934   |
| Philippines   | 1-800-765-7404   |
| Singapore     | 800-886-1028   |
| Taiwan        | 0800-006800  |
| Thailand      | 001-800-886-0010   |
| Fax           | +886-2-2378-6808   |
| Email         | <a href="mailto:tiasia@ti.com">tiasia@ti.com</a> or <a href="mailto:ti-china@ti.com">ti-china@ti.com</a> |
| Internet      | <a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>                       |

**Safe Harbor Statement:** This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as TI or its management "believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

**E093008**

All trademarks are the property of their respective owners.